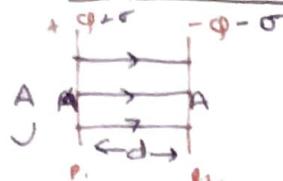


## \* Capacitance \*

### \* Capacitor

$$E = \frac{Q}{\epsilon_0} = \frac{Q}{A\epsilon_0}$$



$$\therefore E = \frac{Q}{\epsilon_0 A}$$

$$\therefore Q \propto V.$$

$$\therefore Q = CV$$

$$C = \frac{Q}{V}$$

unit  $\rightarrow C/V$  or  $F$

$$1F = \frac{1C}{1V}$$

CGS  $\rightarrow$  stat F

$$1F = 9 \times 10^9 \text{ stat-F.}$$

### \* Principle of Capacitor @ Condenser

- Capacity of the conductor is increased by keeping another earth connected conductor near it.


$$V + \begin{array}{c} + \\ | \\ + \\ | \\ + \\ | \\ + \end{array} - \begin{array}{c} - \\ | \\ - \\ | \\ - \\ | \\ - \end{array} \rightarrow C = \frac{Q}{V}.$$

$$-V + \begin{array}{c} + \\ | \\ + \\ | \\ + \\ | \\ + \end{array} - \begin{array}{c} - \\ | \\ - \\ | \\ - \\ | \\ - \end{array} \rightarrow C_1 = \frac{Q}{(V-V')} \downarrow$$

$$\therefore C_1 > C$$

### \* Types of Capacitors

#### ① Parallel Plate Capacitor

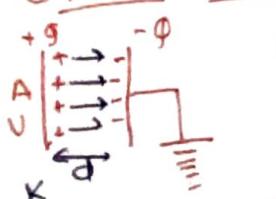

$$E = \frac{Q}{\epsilon_0 K} = \frac{Q}{A\epsilon_0 K}$$

$$E = \frac{V}{d}$$

$$\frac{V}{d} = \frac{Q}{A\epsilon_0 K}$$

$$\therefore \frac{Q}{V} = \frac{\epsilon_0 A K}{d} \quad \therefore C = \frac{\epsilon_0 A K}{d}$$

for air  $K=1$


$$C_a = \frac{\epsilon_0 A}{d}$$

$$K = \frac{C_m}{C_a}$$

$$K = \frac{\epsilon}{\epsilon_0} = \frac{Fa}{F_m} = \frac{Ea}{E_m} = \frac{Va}{V_m} = \frac{Qa}{Q_m} = \frac{C_m}{C_a}$$
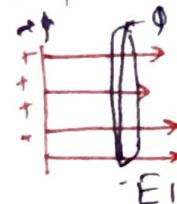
### \* Force b/w two plates of Capacitor

$$F = -\Phi E_i \\ = -\Phi \times \frac{6}{2\epsilon_0} \\ = -\Phi \cdot \frac{Q}{A\epsilon_0}$$



$$F = -\frac{\Phi^2}{2\epsilon_0 A}$$

$$F = \frac{\sigma^2 \cdot A}{2\epsilon_0}$$

$$F = \frac{1}{2} \epsilon_0 E^2 A$$

$$F = \frac{1}{2} \epsilon_0 \frac{V^2}{d^2} A$$

$$\therefore F = \frac{CV^2}{2d}$$

### \* Capacitance of isolated spherical conductor



$$V = \frac{1}{4\pi\epsilon_0} \frac{Q}{R}$$

$$\frac{Q}{V} = 4\pi\epsilon_0 R$$

$$\therefore C = 4\pi\epsilon_0 R$$

$$C = \frac{R}{K}$$


$$C \propto R$$

$$\therefore \frac{C_1}{C_2} = \frac{R_1}{R_2}$$

unit of  $\epsilon_0 \rightarrow$  Farad/meter

$$\rightarrow C_{\text{earth}} = 711 \mu F$$

### \* Spherical Capacitor

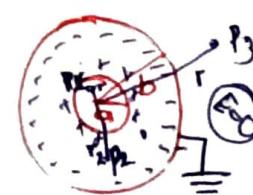

$$\text{At Pt. } P_1, E=0.$$

$$\text{At } P_3, E=0$$

$$\text{At } P_2 \Rightarrow E \neq 0.$$

$$\rightarrow E = \frac{KQ}{r^2}$$

$$\rightarrow E = -\frac{dV}{dr}$$

$$\therefore V = -Edr$$

$$\int dr = \int E dr$$


$$V = -\frac{1}{2} \frac{KQ}{r} \quad \therefore V = \frac{KQ}{2} \frac{1}{r} - \frac{1}{2}$$

$$J = \mu_0 (b-a) / ab$$

$$\frac{q}{V} = \frac{ab}{K(b-a)}$$

$$C = 4\pi\epsilon_0 (ab/ba)$$

\* Cylindrical capacitor.

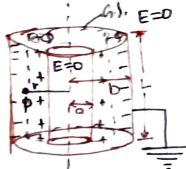

$$E = \frac{1}{2\pi\epsilon_0} \cdot \frac{1}{r}$$

$$E = \frac{1}{2\pi\epsilon_0} \frac{\phi}{d}$$

$$V = \int_E dr = b \int_E dr$$

$$= \frac{1}{2\pi\epsilon_0} \left( \frac{\phi}{r} \right) dr = \frac{\phi}{2\pi\epsilon_0 d} \int_a^b \frac{1}{r} dr$$


$$= \frac{\phi}{2\pi\epsilon_0 d} [\log r]_a^b$$

$$V = \frac{\phi}{2\pi\epsilon_0 d} \log \left( \frac{b}{a} \right)$$

$$\frac{\phi}{V} = \frac{2\pi\epsilon_0 d}{\log(b/a)} \quad C = \frac{2\pi\epsilon_0 d}{\log(b/a)}$$

Cap

\* Energy stored in capacitor.

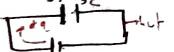

$$\begin{aligned} \phi &= 0 \\ V &= 0 \\ C &\neq 0 \end{aligned}$$

$\boxed{W_T = \frac{1}{2} CV^2}$  by battery.

$$\begin{aligned} dW_T &= dQ \cdot V \\ dW_T &= \frac{q}{C} \cdot V \end{aligned}$$

$$dW_T = dq \cdot dv$$

$$\begin{aligned} dW_T &= \frac{q}{C} dq \\ q &= \frac{1}{C} \int_0^q dq \end{aligned}$$

$$\therefore W = \frac{q^2}{2C}$$

$$\therefore q = CV$$

$$\therefore W = \frac{1}{2} CV^2$$

$$U = \frac{1}{2} \phi V$$

$$\therefore W = U$$

↓  
stored  
in capacitor

$$U = \frac{1}{2} \phi V^2 = \frac{\phi^2}{2C} = \frac{1}{2} \phi V$$

① Battery conn. d

① If separation b/w two plates of capacitor is increased then  
B/w  $\rightarrow$  potential  
difference  $\rightarrow$  decreased.  
Remaining conn.

$$\begin{aligned} ① C &= \frac{A\epsilon_0}{d} \quad [C \propto \frac{1}{d}] \\ C &\text{ decrease} \end{aligned}$$

$$② \phi = \text{const.}$$

$$③ V \rightarrow V \propto \frac{1}{C} \text{ and}$$

$\therefore V$  increase

$$④ E.F. \rightarrow$$

$$E = \frac{1}{d} \frac{\phi}{\epsilon_0}$$

$$E = \frac{1}{d} \frac{V}{\epsilon_0}$$

$$\therefore E = \text{const.}$$

⑤ Energy stored

$$U = \frac{\phi^2}{2C}$$

$$\therefore U = \text{increases}$$

$$⑥ U = \frac{1}{2} CV^2$$

$$\therefore U = \text{decreases}$$

If Dielectric slab of dielectric const. K is introduced betw two plates of capacitor.

Battery

disconn.

① Capacitance

$$C \uparrow$$

②  $\phi$ -charge

$\rightarrow$  const.

$$③ U \rightarrow \phi = CV$$

$$U \propto \frac{1}{C}$$

$\therefore U$  decreases

$$④ E.F. = \frac{U}{d} = \frac{\phi}{\epsilon_0}$$

$$E = \frac{1}{d} \frac{\phi}{\epsilon_0}$$

E = decreases.

$$⑤ U \rightarrow \frac{\phi^2}{2C}$$

$$⑥ U = \frac{1}{2} CV^2$$

$\therefore U$  decreases

$$⑦ U = \text{increased}$$

$$⑧ A metal surface of area 1m<sup>2</sup>$$

is charged with 8.85nC

in air then mechanical force acts

on it  $\downarrow$

$$F = \frac{\phi^2}{2\epsilon_0 d^2}$$

$$= \frac{8.85 \times 9.8 \times 10^{-12}}{2 \times 8.85 \times 10^{-12}}$$

$$= 4.425 N$$

$$⑨ A charge of 6nC is uniformly$$

distributed on surface of a rect.

metallic plate of length 2m

& breadth 1.5m placed in air.

then outward pull on the

plate  $\downarrow$

$$F = \frac{\phi^2}{2\epsilon_0 d^2}$$

$$= \frac{3.6 \times 10^{-12}}{2 \times 8.85 \times 10^{-12}}$$

$$= \frac{0.339}{2.81} = 0.339$$

g. the energy density at a point in a medium of  $K=8$  is  $26.55 \times 10^6 \text{ J/m}^3$ . The electric field

intensity  $E$

$$26.55 \times 10^6 = \frac{1}{2} \frac{e^2}{8} \times K \times E^2$$

$$\frac{e \times 10^{18}}{8} =$$

$$\frac{e^2}{4} \times 10^{18} = E^2$$

$$\therefore E = \frac{\sqrt{3} \times 10^9}{2}$$

g. A circular metal plate of radius 5cm charged with 100nC situated in air then mechanical force acting on 1 side of plate is

$$F = \frac{100 \times 10^{-12}}{8.85 \times 10^{-12} \times 1.5 \times 10^{-2} \times 10^{-2}}$$

$$= \frac{10^6}{8.85 \times 10^{-12}} = \frac{10^6}{8.85} \approx 10^6$$

$$F = \frac{1}{4\pi\epsilon_0 R^2} \frac{Q^2}{2}$$

$$= \frac{8.9 \times 10^9 \times 100 \times 10^{-12}}{4 \pi \times 8.85 \times 10^{-12}}$$

$$= 4 \times 10^8$$

$$= 4000$$

g. A cond. of capacity 4UF is charged to pot. of 300V. If an additional charge of -3x10<sup>-4</sup>C is deposited on it then resultant pot. is

$$\therefore Q = CV = 4 \times 10^{-6} \times 300 = 1200 \times 10^{-6}$$

$$V = 1200 \times 10^{-6} - 3 \times 10^{-4}$$

$$= \frac{3 \times 10^{-4}}{2 \times 10^{-6}} = 2.75 \times 10^2 = 275 V$$

g. A spherical capacitor has an inner sphere of radius 1cm and outer sphere of 10cm radius. The capacitance of capacitor is,

$$\therefore C = \frac{4\pi\epsilon_0}{2} \frac{(ab)}{b-a}$$

$$= 4 \times 8.85 \times 10^{-12} \times \frac{10 \times 1}{10-1}$$

$$= \frac{4 \times 8.85 \times 10^{-12} \times 10}{9} = \frac{4 \times 8.85 \times 10^{-11}}{9} = 4.02 \times 10^{-11}$$

$$= 4.46 \times 10^{-11}$$

Q. What capacitance is required to store an energy of 1000J at a pot. diff. of 10<sup>4</sup>Volt.

$$\rightarrow E = \frac{1}{2} CV^2, \therefore C = \frac{2E}{V^2}$$

$$\frac{2 \times 1000 \times 10^4 \times 3600}{10^8} = 7.2 F$$

Q. Find energy stored in the E.F. produced by a metal sphere of radii R containing charg  $\phi$ .

$$\rightarrow E = \frac{\phi^2}{2C}, C = \frac{\phi^2}{8\pi\epsilon_0 R^2}$$

Q. A metal sphere of 4 cm radius is suspended within hollow sphere of radii 6 cm. The inner sphere charged to pot. of 36V. & outer sphere is earth then charge on inner sphere is.

$$V = \frac{1}{4\pi\epsilon_0} \frac{q(b-a)}{ab}$$

$$\phi = \frac{q}{4\pi\epsilon_0 R^2} = \frac{3}{(4\pi\epsilon_0 \times 10^{-9}) \times 4^2} = \frac{18 \times 10^{-9}}{2.56 \times 10^{-9}}$$

$$\phi = 36 \times 10^{-9}$$

$$C = 4\pi\epsilon_0 \frac{ab}{b-a} = \frac{24}{2} = 12 \text{ pF}$$

$$\phi = CV = 36 \times 10^{-9}$$

Q. A capacitor having capacity of 500PF is charged to pot. of 2000V. If area of each plate of capacitor is 10cm<sup>2</sup> & dist b/w plate is 0.1mm then energy density b/w plate is

$$\rightarrow \phi = \frac{CV}{A \cdot d} = \frac{2000 \times 500 \times 10^{-12}}{10 \times 10^{-4} \times 0.1 \times 10^{-3}} = 10^2$$

$$U = \frac{CV}{V} = \frac{1}{2} CV^2 = \frac{1}{2} \times 500 \times 2000^2 = 10^9 J/m^2$$

what dist apart should 2 plate of area (0.2m<sup>2</sup> x 0.1m) of a PP air capacitor be placed in order to have the same capacitance as spherical cond. of radio 5m

$$\rightarrow \frac{E \cdot A}{d} = \frac{4\pi\epsilon_0 R^2}{d}$$

$$d = \frac{0.2 \times 0.1}{4\pi\epsilon_0 R^2} = \frac{0.1}{8\pi\epsilon_0 \times 5^2} = \frac{0.1}{500} = 2 \times 10^{-3} \text{ m}$$

$$\therefore d = \frac{0.1}{2 \times 10^{-3}} = 50 \text{ mm}$$

Q. If charge on capacitor is increased by 2 coulomb, the energy stored init increased by 21% then original charge on capacitor is

$$\rightarrow E = \frac{\phi^2}{2C}, E \propto \phi^2$$

$$E - 0.21E = (x-2)^2$$

$$1.79E = (x-2)^2 \quad x = \frac{E + \phi^2}{\phi^2}$$

$$\therefore E' = \left(\frac{\phi}{\phi'}\right)^2$$

$$\frac{11}{10} = \frac{\phi+2}{\phi} \quad \therefore \frac{11\phi}{10} = 10\phi + 20 \quad (\phi = 20)$$

\* Combination of charged drops

$$\begin{matrix} n \text{ identical drop} \\ 000 \\ 000 \end{matrix} \quad (B.D.)$$

$$\begin{matrix} \phi q \\ C \\ r \\ \sigma \\ V \\ U \end{matrix} \quad \begin{matrix} \phi' \\ C' \\ r' \\ \sigma' \\ V' \\ U' \end{matrix}$$

① Charge ( $\phi$ )  
( $\phi = nq$ )

② Radius ( $r$ )

$$V_{B,D} = nV_{S,D}$$

$$\frac{4}{3}\pi r^3 = n \times \frac{4}{3}\pi r^3$$

$$\therefore R = \sqrt[3]{n} r$$

③ Capacitor inc

$$C \propto R$$

$$\therefore C = nV^2 C$$

④ Surface charge density.

$$\sigma' = \frac{\phi}{4\pi r^2}$$

$$\sigma' = n^{1/3} \sigma$$

⑤ Potential ( $V$ )

$$V = C'V'$$

$$V' = \frac{\phi}{C'}$$

$$= \frac{nq}{n^{1/3} C}$$

$$V' = n^{2/3} V$$

⑥  $V'$

$$V' = \frac{1}{2} C' V'^2$$

$$V' = \frac{1}{n^{4/3}} V$$

$$U' = n^{5/3} U$$


\* Grouping of capacitor.

① Series capacitor grouping

$\Rightarrow$  same  
v = dibb

$$U = U_1 + U_2 + U_3$$
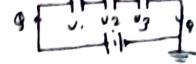
$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



②  $C_S < C_1 / C_2 / C_3$

③ Series comb' → capacitance less

$$\Rightarrow U = \frac{\phi}{C} \rightarrow \text{same} \quad U = V \propto \frac{1}{C} \downarrow$$

$$\therefore \frac{U_1}{U_2} = \frac{C_2}{C_1}$$


④ For  $n$  identical capacitor

$$C_S = \frac{C}{n}$$

$$\begin{matrix} C_1 & C_2 \\ || & || \\ V & U \end{matrix} \quad U = \sqrt{\frac{C_2}{C_1 + C_2}}$$

$$U_2 = U \left[ \frac{C_1}{C_1 + C_2} \right]$$

⑤ Parallel grouping

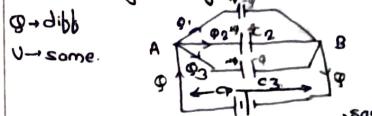

$$\phi = \phi_1 + \phi_2 + \phi_3$$

$$C_P = C_1 + C_2 + C_3$$

$$C_P > C_1 / C_2 / C_3$$

⑥ Parallel comb' = capacitance less

$\Rightarrow C = C_U$

$$\therefore \frac{\phi_1}{\phi_2} = \frac{C_1}{C_2}$$

⑦ For  $n$  identical capacitor

$$C_P = nC$$

$$\begin{matrix} C_1 & C_2 \\ || & || \\ 0 & 0 \end{matrix} \quad U = \sqrt{\frac{C_2}{C_1 + C_2}} \cdot U$$


$$\phi_1 = \phi \left[ \frac{C_1}{C_1 + C_2} \right]$$

$$\phi_2 = \phi \left[ \frac{C_2}{C_1 + C_2} \right]$$

\* Group of plates.
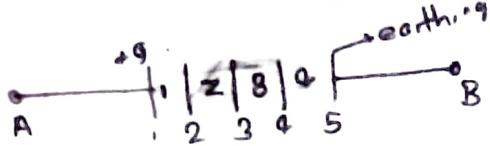
### ① Series

→ If  $n$  no. of plates are arranged one after another b/w two pts as shown in fig then  $(n-1)$  capacitor will form & they will be in series grouping.




$$C_s = \frac{C}{n-1}$$

$$C_s = \frac{A\epsilon_0}{(n-1)d}$$


$$C_{AB} = \frac{C}{4} = \frac{A\epsilon_0}{4d}$$
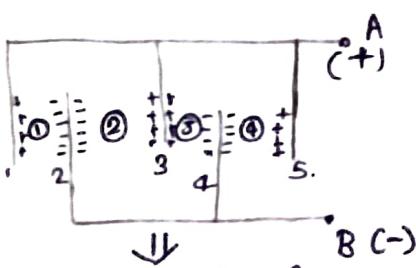
### ② Parallel



→ If  $n$  no. of plates are arranged b/w two points such that even no. of plates are conn. together and odd no. of plate conn. together then  $(n-1)$  capacitor will be formed and they will be in parallel grouping.



$$C_s = 4C = \frac{4A\epsilon_0}{d}$$

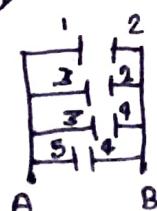

$$C_s = \frac{(n-1)\epsilon_0 A}{d}$$

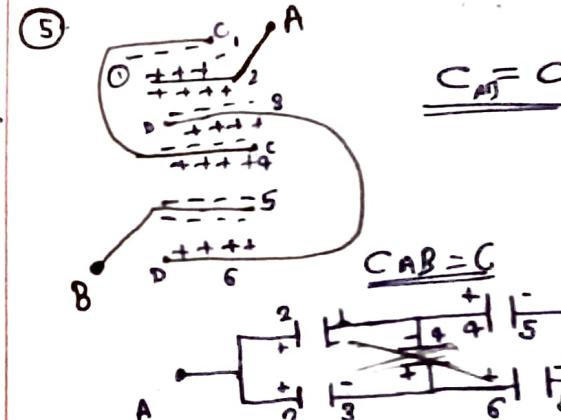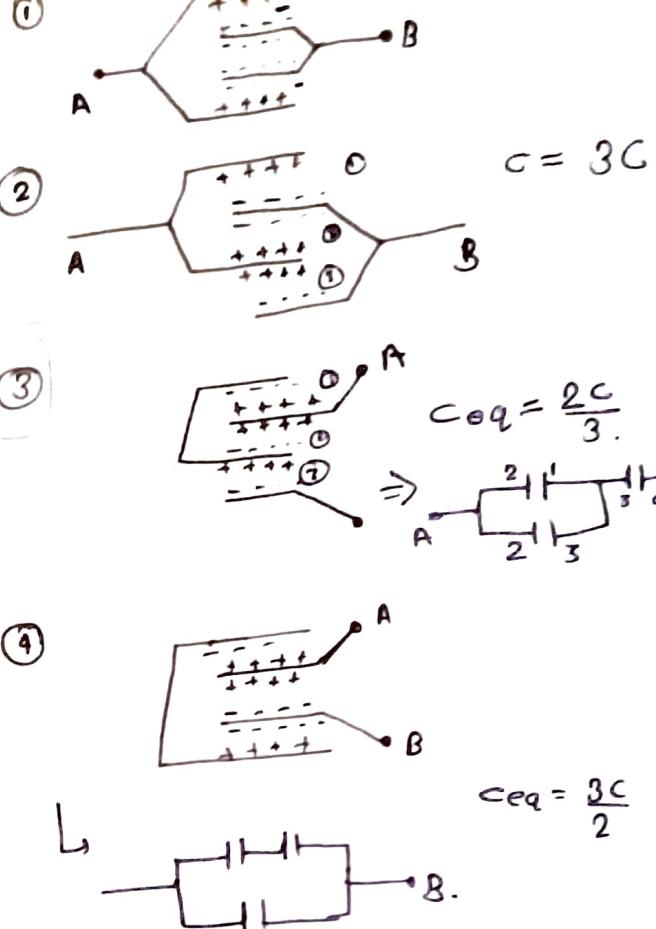

③ In circuit shown in fig. The total charge is  $\pm 50 \mu C$  then value of  $V_1$ ,  $V_2$ ,  $C_1$ ,  $C_2$ ,  $C_3$  resp. are.

$C_{eq}$ ,


$$Q = CV$$

$$750 = 15 \mu F \times V$$

$$\therefore V_1 = \frac{750}{15} = 50 V$$

$$V = V_1 + V_2 = 70 V$$






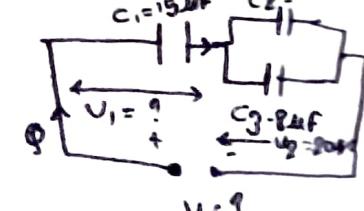
$$\therefore Q_3 = V_2 C_3 \\ = 160 \mu C$$



$$C = \frac{Q}{V} = \frac{50}{50} = 1 \mu F$$



Q. The eq. capacitance betn A & B is

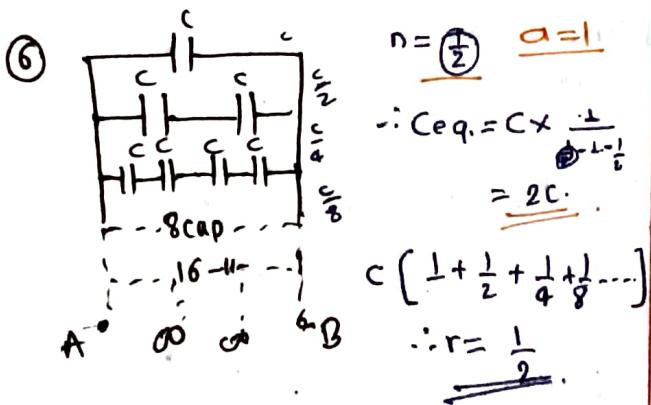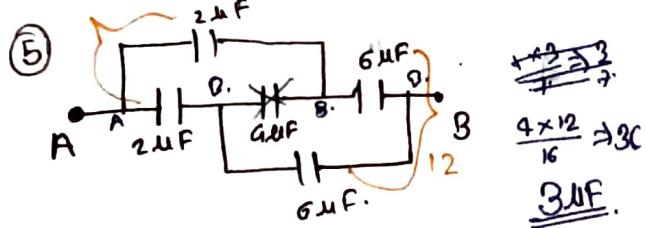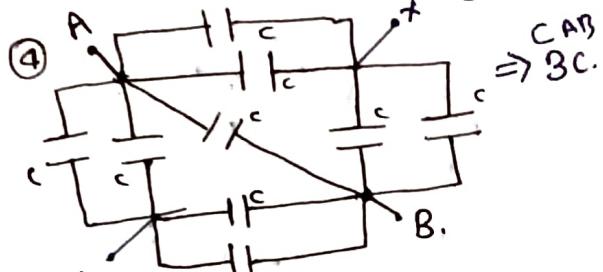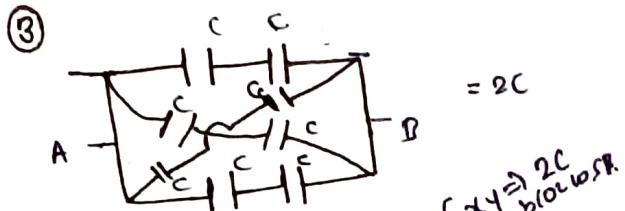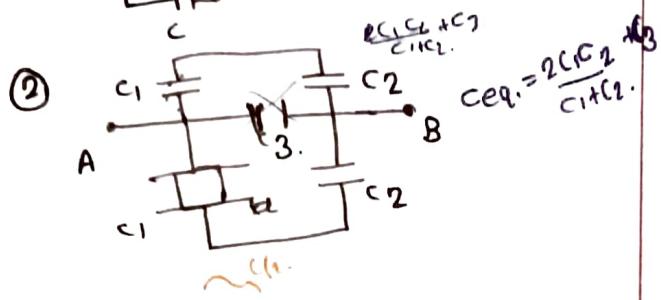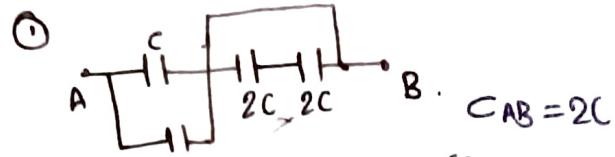


Q. In circuit shown in fig. the charge on 12μF capacitor is

$$C_{eq} = 5\mu F$$

$$\Phi = 5\mu F \times 600$$

$$= 2000 \mu C.$$

$$= 2 mC.$$

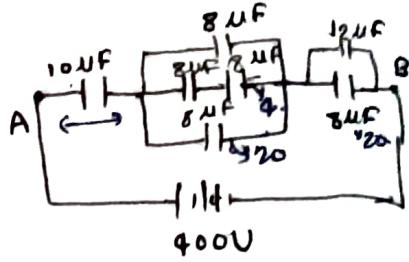


$$\Phi_{12} = \left( \frac{12}{20} \right) \times 2 \times 10^3$$

$$= \frac{12 \times 10^3}{10} mC$$

$$= 1200 \mu C.$$

Q. A gang capacitor is formed by interlocking a number of plates as shown in fig. The dist. betn plate is 0.885cm and overlapping area of plate is 5cm<sup>2</sup> then capacity of gang capacitor is
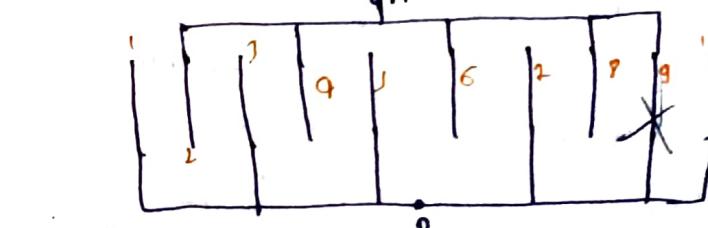
$$\frac{E_0 A}{d} \Rightarrow \frac{8.85 \times 10^{-12} \times 5 \times 10^{-4}}{0.885 \times 10^{-2}} = 5 \times 10^{-13} F$$




$$C = (n-1) C$$

$$= 8C$$

$$\therefore 8 \times 5 \times 10^{-13} \Rightarrow 4 \times 10^{-12} F$$

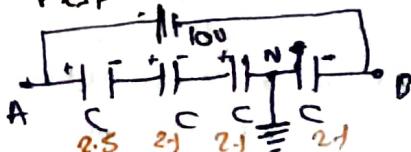Q. Four identical capacitor are conn. in series with 10V battery as shown in figure then pot. at pt. A and at pt. B resp. are.




$$V_A - V_N = 2.5 + 2.5 + 2.5$$

$$V_A = 7.5V$$


~~$$V_N - V_B = 2.5$$~~

~~$$V_B = -2.5V$$~~

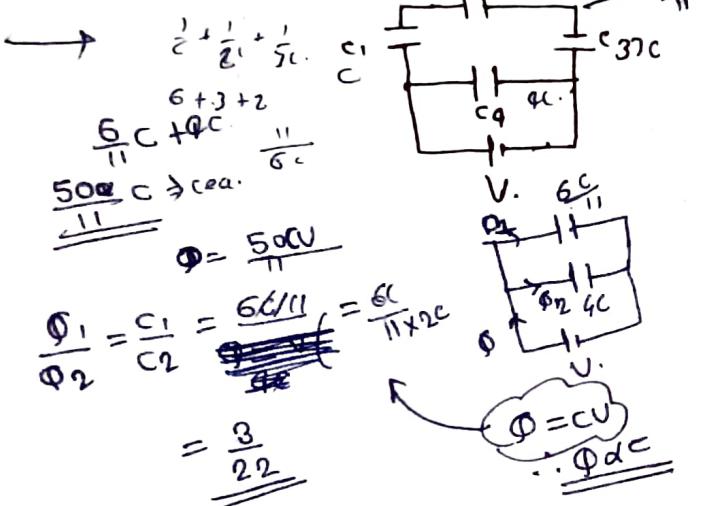A Network of 4 capacitor of capacity equal to  $C_1 = C$ ,  $C_2 = 2C$ ,  $C_3 = 3C$ ,  $C_4 = 4C$  are conn. to battery as shown in figure then ratio of charges on  $C_2$  &  $C_4$  is -



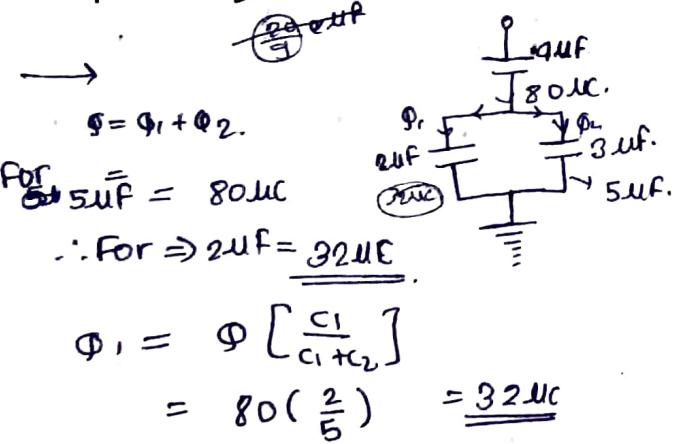Q. In given circuit a charge of  $80\mu\text{C}$  is given to upper plate of  $4\mu\text{F}$  capacitor then charge on lower plate of  $2\mu\text{F}$  is -




Q. Two concentric spherical metal shell of radii  $a$  &  $b$  ( $b > a$ ). The outer shell has charge  $\Phi$ . If inner shell grounded then charge appear on inner shell is

$\rightarrow$  ~~ind.~~ only inner to outer.



$$V_p = K \left[ \frac{\Phi + q}{b} \right] \quad V_p = 0$$
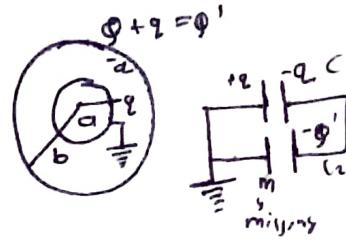
$$\therefore \frac{\Phi}{b} = \frac{q}{a} \quad \therefore q = -\frac{\Phi a}{b}$$



$$C_1 = 4\pi\epsilon_0 \left( \frac{ab}{b-a} \right)$$

$$C_2 = 4\pi\epsilon_0 b.$$


$$\therefore C_{eq.} = C_1 + C_2 = 4\pi\epsilon_0 \left( \frac{ab}{b-a} + b \right)$$

$$C_{eq.} = 4\pi\epsilon_0 \left( \frac{b^2}{b-a} \right)$$

Inner sphere grounded.

Q. The eq. capacitance betn A & B is.
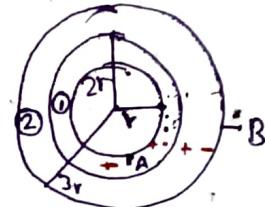
$$\rightarrow C_1 = 4\pi\epsilon_0 \left( \frac{2r^2}{r} \right) = 4\pi\epsilon_0 2r.$$




$$C_2 = 4\pi\epsilon_0 \left( \frac{6r^2}{r} \right) = 4\pi\epsilon_0 6r$$

$$C_{eq.} = \frac{2C}{3} = \frac{2}{3} \times 4\pi\epsilon_0 2r \frac{2C}{3}$$

$$C_{eq.} = \frac{3C}{4}$$


Q. ~~Induced~~ induced ~~capacitance~~  $\Phi$  is divided by  $n$

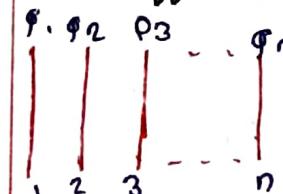Q. The charge given to the isolated plates of large surface area, as shown in fig. The capacitance betn adjacent plate is  $C$ . Then pot. diff. betn plates 1 & 2 is.



$$\Phi_T = \Phi_1 + \Phi_2 + \Phi_3 + \dots + \Phi_n$$
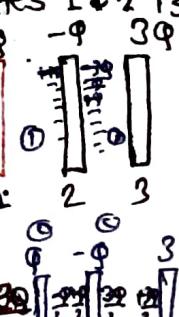
$$\therefore \Phi_{outer} = \frac{\Phi_T}{2}$$



$$V_{12} = \frac{\Phi}{2C} = \frac{\Phi}{2C}$$

$$V_{23} = \frac{3\Phi}{2C}$$

$$\Phi_{outer} = \frac{3\Phi}{2}$$



Two condenser of capacities  $4\text{ mF}$  &  $8\text{ mF}$  are charged to  $200\text{ V}$  &  $150\text{ V}$  resp. Then common pot. when they are conn. in parallel.

$$V_C = \left[ \frac{\Phi_1 + \Phi_2}{C_1 + C_2} \right] = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

$$= \frac{4 + 8}{12} = \frac{80 + 120}{120 \text{ mF}}$$

$$= \frac{200}{12} = \frac{100}{6} = \underline{\underline{\frac{50}{3} \text{ V}}}$$

Q. A  $5\text{ mF}$  capacitor is fully charged across a  $120\text{ V}$  battery and then conn. to an uncharged capacitor. The voltage across it is found to be  $3\text{ V}$ . Then capacity of uncharged capacitor is

$$\rightarrow 3 = \frac{60 + C_2 \cdot 0}{C_1 + C_2}$$

$$15 + 3C_2 = 60$$

$$3C_2 = 45$$

$$C_2 = \underline{\underline{15 \text{ mF}}}$$

Q. Two insulated metallic spheres of  $3\text{ mF}$  &  $5\text{ mF}$  capacitance are charged to  $300\text{ V}$  &  $500\text{ V}$  resp. When they are joined by wire then energy loss is

$$\rightarrow \Delta U = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} [U_1 - U_2]$$

$$= \frac{1}{2} \times \frac{15 \text{ mF}}{8 \text{ mF}} [-200]$$

$$= \frac{1500 \times 10^{-6}}{8} = \frac{1.5}{8} \times 10^{-3}$$

Q. A  $10\text{ mF}$  capacitor &  $20\text{ mF}$  capacitor are conn. in series across  $200\text{ V}$  supply. The charge capacitors are then disconn. from supply and reconnected with their +ve plate together & -ve plate together & no ext. volt is applied then pot. diff. across each capacitor is

$$\rightarrow \text{Series} \rightarrow V_1 = 200 \left( \frac{20}{30} \right)$$

$$= \frac{400}{3} \times 10^{-6}$$

$$V_2 = \frac{200}{3} \times 10^{-6}$$

$$V_C = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{10 \times 10^{-6} \times \frac{400}{3} \times 10^{-6} + \frac{200}{3} \times 10^{-6}}{30}$$

$$= \frac{600}{90}$$

$$C_S = \frac{C_1 C_2}{C_1 + C_2} = \frac{20}{3} \text{ mF}$$

$$\Phi = C V = \frac{20}{3} \times 200 \Rightarrow \frac{4000}{3}$$

$$= \frac{4000}{3} \text{ mC} = \Phi_1 = \Phi_2 = \Phi$$

$$V_C = \frac{\Phi_1 + \Phi_2}{C_1 + C_2}$$

$$= \frac{\frac{4}{3} + \frac{4}{3}}{30} = \frac{\frac{8}{3} \times 10^{-3}}{3 \times 30 \times 10^{-6}}$$

$$= \frac{8000}{90} = \underline{\underline{88.8 \text{ V}}}$$

Q. A  $20\text{ F}$  capacitor is charged to  $5\text{ V}$  & isolated. It is then conn. in parallel with an uncharged  $50\text{ F}$  capacitor. Then dec. in energy of system will be

$$\rightarrow \Delta U = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} [U_1 - U_2] = \frac{1}{2} \frac{100}{50} = 2 \text{ J}$$

$$\Delta U = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} [U_1 - U_2]$$

$$= \frac{1}{2} \times \frac{600}{50} \times [5]^2 = \underline{\underline{150 \text{ J}}}$$

Q. Two isolated met. sphere of radii  $r$  &  $2r$  are charged such that both of these have same surface charge density  $\sigma$ . The sphere are conn. by thin cond. wire then the new charge density on bigger sphere is,

$$\rightarrow \frac{\Phi_1}{4\pi r^2} = \frac{\Phi_2}{4\pi (2r)^2}$$



$$\sigma_1 = \frac{\Phi_2}{4}$$

$$\sigma_2 = 4\sigma_1$$

$$\underline{\underline{\sigma}}$$

$$\sigma_2' = (\sigma_1 + \sigma_2) \frac{r_2}{r_1 + r_2}$$

$$= 5\sigma_1 \frac{2r}{3r}$$

$$= \frac{10\sigma_1}{3}$$

$$\sigma_2' = \frac{10\sigma_1}{3 \times 4\pi (2r)^2}$$

$$= \frac{10\sigma_2}{12 \times 4\pi (2r)^2}$$

$$\sigma_2' = \sigma_2 = 5\sigma_1 \frac{r}{3r} = \frac{5\sigma_1}{3}$$

$$= \frac{5}{6} \sigma_1$$

## \* Dielectric and Polarisation

Polar

$\rightarrow$  C.O.M. of +ve charge doesn't coincide with -ve charge C.O.M.

$$\rightarrow \text{(+ -)}$$

$\rightarrow$  shape unsymm.

$$\rightarrow (\vec{P} = q\vec{l} = 10^{-30} \text{ cm})$$

$$\rightarrow \text{eg: HCl, H}_2\text{O}$$

Non-polar

$\rightarrow$  C.O.M. of +ve charge coincides with C.O.M. of -ve charge.

$$\rightarrow \text{(+ +)}$$

$\rightarrow$  shape-symm.

$$\rightarrow \vec{P} = 0$$

$$\rightarrow \text{eg: O}_2, \text{H}_2, \text{N}_2, \text{CH}_4, \dots$$

① Behaviour of Non-polar dielectric in ext. electric Field.

a) In absence of E.F.

$$\vec{E} = 0$$

$$\vec{P} = 0$$

$$P_{\text{net}} = 0$$




b) In presence of E.F.



$$\rightarrow \vec{E} \neq 0$$

$$\rightarrow P_{\text{e.m.}} \neq 0$$
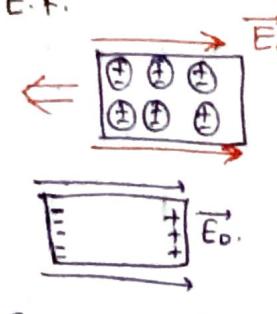
$$(P_{\text{net}})_{\text{sub}} \neq 0.$$



(e.m. = each mol.)

\* electric Polarization.

The process of inducing eq. and opp. charge on two opp. faces of dielectric is called electric polarization.

② Polar dielectric in ext. e.f.

a) In absence of E

$$\vec{E} = 0.$$

$$P_{\text{e.m.}} \neq 0$$

$$P_{\text{net}} = 0$$




b) In presence of E

$$\vec{E} \neq 0$$

$$P_{\text{e.m.}} \neq 0$$
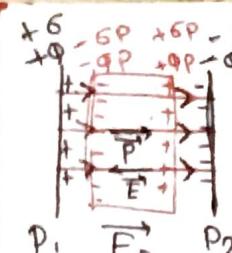
$$(P_{\text{net}})_{\text{sub}} \neq 0.$$



$$\epsilon_0 = \frac{\sigma}{\epsilon_0}$$

$$E_p = \frac{\sigma_p}{\epsilon_0}$$

$$E_{\text{net}} = \frac{1}{\epsilon_0} [\epsilon - \epsilon_p]$$

$$E_{\text{net}} = \frac{1}{\epsilon_0} [\epsilon - \epsilon_p]$$

$$\frac{\sigma}{\epsilon_0 k} = \frac{1}{\epsilon_0} \epsilon - \epsilon_p$$

$$K = \frac{\sigma}{\epsilon - \epsilon_p} \rightarrow \text{SIC} \rightarrow \text{specific inductive capacitance.}$$

$$K\epsilon - K\epsilon_p = \sigma$$

$$\sigma(k-1) = K\epsilon_p$$

$$\epsilon_p = \sigma [1 - \frac{1}{k}]$$

$$\sigma_i = \sigma [1 - \frac{1}{k}]$$

$$\phi_i = -\epsilon [1 - \frac{1}{k}]$$

\* Polarization Density  $[\vec{P}]$  :-

↑  $P_{\text{net}} \propto \text{Volume}$

$$\vec{P}_{\text{net}} = \vec{P} \cdot V$$

$$\vec{P} = \frac{P_{\text{net}}}{V} \quad [\text{TAL}^2]$$

$$P_{\text{net}} = \Phi_p \cdot d$$

$$V = A \cdot d$$

$$\vec{P}_{\text{net}} = \frac{\Phi_p}{V} = \vec{P} = \sigma_p \cdot V$$

$$\vec{P} = \sigma V$$

\* Electric Susceptibility. ( $\chi_e$ )

$$\vec{P} \propto \vec{E}_R \rightarrow \text{reduced E.F.}$$

$$P = \chi_e \vec{E}_R E_0$$


$$\chi_e = \frac{\vec{P}}{\vec{E}_R E_0}$$

## Effect of dielectric on capacitance

$$\rightarrow E_0 = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0}$$


$$\rightarrow V_0 = Ed.$$
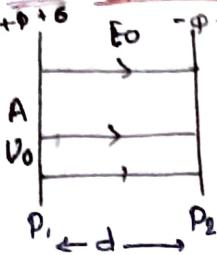
$$\rightarrow C = \frac{\epsilon_0 A}{d}$$



→ Two plate joined by another plate.
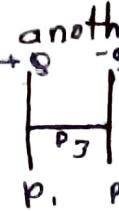
$$\therefore C = \frac{Q}{V_0} = \frac{\infty}{\epsilon_0}$$



$$\rightarrow E_m = \frac{\epsilon_0}{K}$$

$$\rightarrow t = E_m$$

$$\rightarrow (d-t) = E_0$$


$$\rightarrow V = (d-t)E_0 + t(E_m)$$

$$V = \epsilon_0 [(d-t) + \frac{t}{K}]$$

New p.d.  
betn  
two plate.

$$V = \frac{\epsilon_0}{\epsilon_0 A} [d-t] + \frac{t}{K}$$
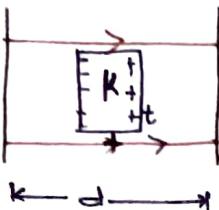
$$\therefore C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{K}}$$



→ If entire space betw two capacitor is filled with dielectric then capacitance is

$$\rightarrow t=d.$$

$$\therefore C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{K}}$$

$$\therefore C = \frac{\epsilon_0 A K}{d}$$

→ If several dielectric slab of dielectric const.  $K_1, K_2, K_3, \dots$  with their resp. thickness  $t_1, t_2, t_3, t_4, \dots$  fill completely betw two plate of capacitor then new capacitance is

$$C = \frac{\epsilon_0 A}{\frac{t_1}{K_1} + \frac{t_2}{K_2} + \dots}$$

$$d = t_1 + t_2 + t_3 + \dots$$

→ If dielectric slab is replaced by cond. slab thickness  $t$  then new capacitance is

$$C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{K}}$$

$$\therefore C = \frac{\epsilon_0 A}{(d-t)}$$

Q. A PPC partially filled with dielectric plate of thickness 6 mm & ~~K=3~~ K=3. The area of plate of capacitor is  $2 \times 10^{-3} \text{ m}^2$  & dist. b/w plate is 0.01m then capacitance of capacitor  
→ d=10mm

$$C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{K}} = \frac{\epsilon_0 \times 2 \times 10^{-3}}{4 \times 10^{-3} + \frac{6}{3} \times 10^{-3}}$$

$$C = \frac{\epsilon_0 \times 2}{\epsilon} = \frac{\epsilon_0}{3}$$

Q. The A of plate of PPC is A & the dist. b/w plate is 10mm there are 2 dielectric sheet in it one of dielectric const.  $\frac{1}{10}$  &  $t=6\text{mm}$  & other of  $K=5$  &  $t=4\text{mm}$  find capacitance

$$\rightarrow C = \frac{\epsilon_0 A}{\frac{t_1+t_2}{K_1+K_2}} = \frac{\epsilon_0 A}{\frac{6+4}{10+5}} = \frac{10 \epsilon_0 A}{15}$$

$$\therefore \frac{5 \epsilon_0 A \times 10^3}{7}$$

Q. If dielectric plate of thickness  $t$  is introduced b/w plate of capacitor of dist.  $d$ , the capacitance become half. Then original value of dielectric const. of plate is,

$$\rightarrow C_1 = \frac{\epsilon_0 A}{d}$$

$$C_2 = \frac{C_1}{2} = \frac{\epsilon_0 A}{(d-t) + \frac{t}{K}}$$

$$\therefore \frac{C_1}{C_2} = \frac{(d-t) + \frac{t}{K}}{d}$$

$$2d = (d-t) + \frac{t}{K}$$

$$d = \frac{t}{K} - t$$


Q. The capacitance of capacitor is  $10\text{ nF}$  without dielectric,  $K=2$  is used to fill half dist. b/w plate then find new  $C$ .

$$\rightarrow C_0 = \frac{\epsilon_0 A}{d}$$

$$C_2 = \frac{\epsilon_0 A}{(d - \frac{d}{2}) + \frac{3d}{4}} = \frac{\epsilon_0 A}{\frac{5d}{4}}$$

$$C_2 = \frac{\epsilon_0 A}{\frac{d}{2} + \frac{d}{4}} = \frac{4 \epsilon_0 A}{3d} = \frac{40}{3} \text{ nF.}$$

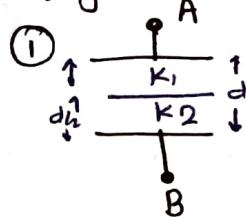Q. A capacitor is filled with two dielectric of same dimension but of dielectric const.  $K_1$  &  $K_2$  resp. Then Capacitance b/w two possible arrangement shown in fig. is.




$$C_1 = \frac{A \epsilon_0}{(\frac{d-d}{2}) + \frac{d}{2/K_1}} = \frac{A \epsilon_0}{\frac{d}{2} + \frac{d}{2K_1}}$$

$$C_2 = \frac{\epsilon_0 A}{\frac{d-d}{2} + \frac{d}{2K_2}} = \frac{\epsilon_0 A}{\frac{d}{2} + \frac{d}{2K_2}}$$


dist. halved  
divide  
arrange in  
series.
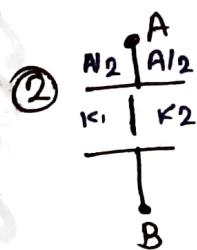
$$C_{AB} = \frac{\epsilon_0 A}{d} \left[ \frac{K_1 K_2}{K_1 + K_2} \right]$$



Area divide  $\rightarrow$  parallel
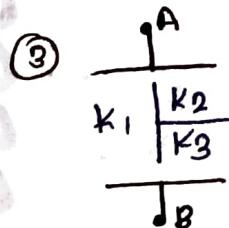
$$C_{AB} = \frac{\epsilon_0 A}{2} [K_1 + K_2]$$



$K_2, K_3$  in series &  
 $K_1$  in parallel.

$$C_{AB} = \epsilon_0 A \left[ \frac{K_2 K_3}{K_2 + K_3} + \frac{K_1}{2} \right]$$

Q. A slab of material of dielectric  $K$  has same area as the PPC has thickness  $3d/4$ , where  $d$  is sep. of plate the ratio of capacitance  $C$  to  $C_0$ .

$$\rightarrow C_0 = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{\frac{d}{4} + \frac{3d}{4K}}$$

$$C = \frac{\epsilon_0 A}{\frac{d}{4}(1 + \frac{3}{K})}$$

$$\therefore C = \frac{4 \epsilon_0 A}{d(1 + \frac{3}{K})} = \frac{4 C_0}{(1 + \frac{3}{K})}$$

$$\therefore \frac{C}{C_0} = \frac{4}{(1 + \frac{3}{K})} = \frac{4K}{K+3}$$

Q. A PPC is maintained at certain pot. diff. when 3mm slab is introduced b/w the plate in order to maintain same p.d. distance b/w plate is increased by 204mm then dielectric const. of slab.

$$\rightarrow \frac{\epsilon_0 A}{d} = \frac{\epsilon_0 A}{(d + 2.4 - 3) + d}$$

All electro.

$$9. \rightarrow \text{take } U' = U \left[ \frac{C_2 C_3}{C_1 C_2 + C_2 C_3 + C_1 C_3} \right]$$

$$59. E = \frac{6 \cdot 10^4}{\epsilon_0 K}$$

$$\sigma = \epsilon_0 K E$$

$$= 8.8 \times 10^{-12} \times 2.2 \times 3 \times 10^4 \\ = 6.3 \times 10^{-7} \text{ C/m}^2$$

$$25. \text{ इतना स्थिति } \frac{\epsilon_0 A}{2d} [K_1 + K_2]$$

34.  $\rightarrow \frac{5}{6} C$  से भी जारी उसमें 3लटा  
bcz यह series parallel हो जाएगा।

$$44. \frac{3+d+2.4-3}{K} = d$$

$$-0.6 = -\frac{3}{K}$$

$$K = \frac{3}{0.6} \quad K = \underline{5}$$

89. देख Area नहीं है  $\therefore \frac{1}{2} QV \rightarrow \text{energy.}$